

23 Series and Parallel Circuits

1. Three $25.0\text{-}\Omega$ resistors are connected in series across a 60.0-V battery.
 - a. What is the equivalent resistance of the circuit?
 - b. What is the current in the circuit?
 - c. What is the voltage drop across each resistor?
2. A string of 36 identical holiday lights is connected in series to a 120-V source. The current through the bulbs is 0.40 A .
 - a. What is the equivalent resistance of the light string?
 - b. What is the resistance of each bulb?
 - c. What power is dissipated by the light string?
3. A lamp with a resistance of $8\text{ }\Omega$ is connected across a 24-V battery.
 - a. What is the current through the lamp?
 - b. What resistance must be connected in series with the lamp to reduce the current to 1.6 A ?
4. A $12\text{-}\Omega$ resistor and a $28\text{-}\Omega$ resistor are connected in series across a battery. The current in the circuit is 0.90 A .
 - a. What is the voltage of the battery?
 - b. What is the voltage drop across the $12\text{-}\Omega$ resistor?
5. Three resistors are connected in series across a 75-V potential difference. R_1 is $170\text{ }\Omega$ and R_2 is $190\text{ }\Omega$. The potential difference across R_3 is 21 V .
 - a. Find the current in the circuit.
 - b. Find the resistance of R_3 .
6. A 15-V battery and two resistors, R_B of $36\text{ }\Omega$ and R_A of $84\text{ }\Omega$, are connected as a voltage divider. What is the voltage across the 36-W resistor?
7. Maria is designing a voltage divider using a 30.0-V battery and a $375\text{-}\Omega$ resistor as R_B . What resistor should be used as R_A if the output voltage across R_B is to be 22.5 V ?
8. A $25\text{-}\Omega$ resistor, a $55\text{-}\Omega$ resistor, and a $75\text{-}\Omega$ resistor are connected in parallel and placed across a 9.0-V battery.
 - a. What is the equivalent resistance of the parallel circuit?
 - b. What is the current through the entire circuit?
 - c. What is the current through each branch of the circuit?
9. Suppose that the $25\text{-}\Omega$ resistor in problem 8 is replaced by a $45\text{-}\Omega$ resistor. Without performing any calculations, describe qualitatively the change in each of the following.
 - a. the equivalent resistance of the parallel circuit
 - b. the current through the entire circuit
 - c. the current through each branch of the circuit

23 Series and Parallel Circuits

10. Two resistors, one $130\ \Omega$ and the other $210\ \Omega$, are connected in parallel. The resistors are then connected to a battery. If the current through the entire circuit is $0.31\ \text{A}$, what is the voltage of the battery?
11. Resistors R_1 , R_2 , and R_3 are connected in parallel. R_1 is $68\ \Omega$ and R_2 is $93\ \Omega$. The equivalent resistance of the parallel combination is $26\ \Omega$. What is the resistance of R_3 ?
12. Four identical resistors are connected in parallel. The equivalent resistance of the parallel combination is $4.5\ \Omega$. What is the resistance of each resistor?
13. A 120-V household circuit that contains a 320-W television, a $1.0 \times 10^2\text{-W}$ lamp, and a 1350-W heater is connected to a $2.0 \times 10^1\text{-A}$ fuse. Will the fuse melt if all three devices are operating simultaneously? Explain.
14. Resistors R_1 , R_2 , and R_3 have resistances of $37.0\ \Omega$, $22.0\ \Omega$, and $41.0\ \Omega$ respectively. R_1 and R_2 are connected in series, and their combination is in parallel with R_3 . This arrangement is then placed across a 60.0-V battery.
 - a. Draw the circuit diagram.
 - b. What is the equivalent resistance of the three resistors?
 - c. What is the current in the circuit?
 - d. What is the current through R_3 ?
 - e. What is the potential difference across R_1 ?
15. A $19\text{-}\Omega$ resistor is connected in series to a 45-V battery and two $12\text{-}\Omega$ resistors that are connected in parallel to each other.
 - a. Draw the circuit diagram.
 - b. What is the equivalent resistance of the three resistors?
 - c. What is the current in the circuit?
 - d. What is the current through one of the $12\text{-}\Omega$ resistors?
 - e. What is the potential difference across the $19\text{-}\Omega$ resistor?